

# Week 3 Report

## ECE 432 Microwave Circuit Design II

Jackson Pugh  
Portland State University  
Portland, OR 97207  
Email: japugh@pdx.edu

Michael Woodruff  
Portland State University  
Portland, OR 97207  
Email: michael.woodruff@pdx.edu

### I. INTRODUCTION

### II. QUESTIONS & ANSWERS

1. Read in one of the S-parameters datafiles for SAV-541+ and plot the frequency dependence of S21, S11 and K (use dB plot). In which region is it unconditionally stable: i.e. where is  $K > 1$  and  $|\Delta| < 1$ , or  $\mu > 1$ ? (one of criteria is sufficient)

Looking at Figure 1, the region where  $\mu > 1$  is: 3.76 - 10.35 GHz.

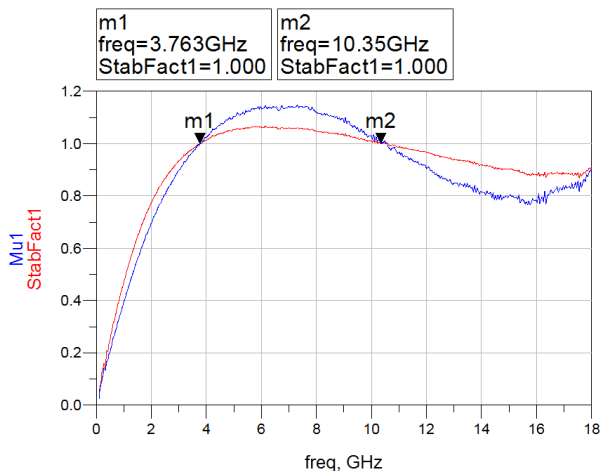


Fig. 1. Plot of  $\mu$  and StabFact (K) from S2P manufacturer data. Transistor stability region is inside the two markers.

2. Pick one frequency at which SAV-451+<sup>1</sup> is unconditionally stable and design input and output matching for maximum transducer gain (simultaneous conjugate match). Construct the circuit in ADS and verify your "hand" calculation. Plot the values of gain and of  $|S21|^2$  for the device alone around some (narrow) frequency range around the center frequency. Comment on your results.

Choose 6 GHz:

Looking at Table I which was provided from the manufacturer S2P file, lists the S-Parameters at approximately 6 GHz. These were used to calculate  $\Gamma_{MS}$  and  $\Gamma_{ML}$ , which are listed in Table II<sup>2</sup>.  $\Gamma_{MS}$  and  $\Gamma_{ML}$  were plotted on the Smith Chart

and then were matched using an open-stub matching network. Figure 4 shows the values of gain and  $|S21|^2$  for the device.

TABLE I. S-PARAMETERS

S-Parameter	Magnitude	Angle (°)
S11	0.70750	93.98
S21	2.57416	-6.897
S12	0.11976	-5.765
S22	0.23939	105.25

TABLE II. REFLECTION COEFFICIENT

Reflection Coefficient	Magnitude	Angle (°)
$\Gamma_{MS}$	0.834	97.80
$\Gamma_{ML}$	0.468	135.13

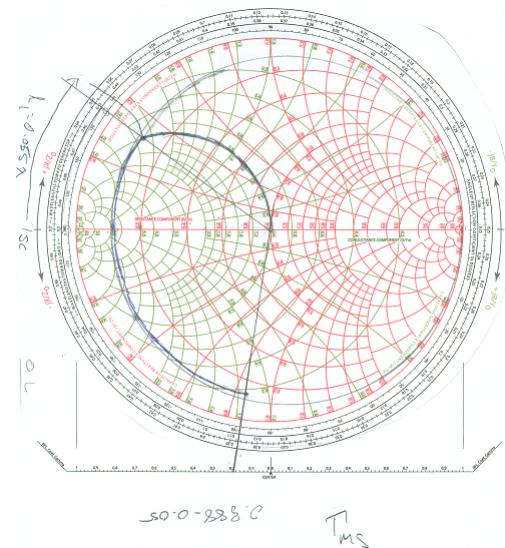


Fig. 2. Input reflection coefficient Smith Chart. Matching network using an open-circuit stub is overlaid the Smith Chart.

3. If you are restricted to values available from IEEE store, what are the values and what will happen to the match? Here is a list of what they are supposed to have:

- a. Inductors: 1.3, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22 nH
- b. Capacitors: 1, 1.3, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 33 pF

If the components are not exact, then the conjugate matching network will not be as effective and there will be non-zero reflection at the ports

<sup>1</sup>SAV-541+

<sup>2</sup>ADS also was able to calculate  $\Gamma$  automatically

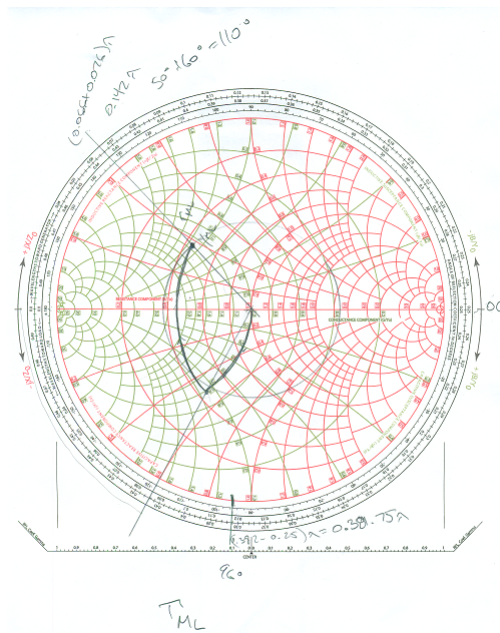


Fig. 3. Output reflection coefficient Smith Chart. Matching network using an open-circuit stub is overlaid the Smith Chart

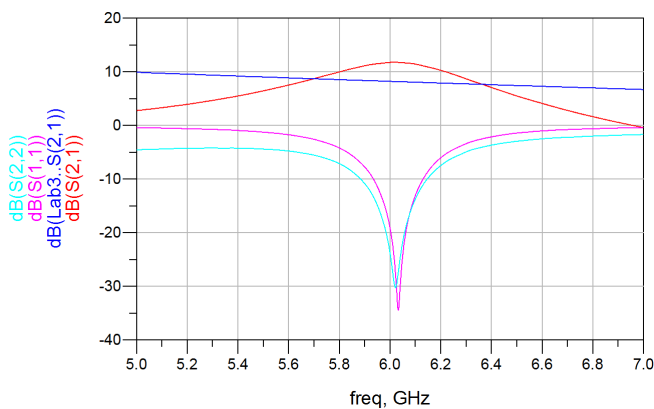


Fig. 4. Plot of S-Parameters after matching network is added.

4. Construct input and output stability circles at 2.4 GHz. Use these results to determine resistance to be placed in shunt on output that would make the device unconditionally stable. (a quick way to do this in ADS will be demonstrated).

Figure 5 shows the input and output stability circles at 2.4 GHz. A rough resistor shunt resistor value on the output to make the device unconditionally stable is 125  $\Omega$ . Optimizing this resistor in ADS gives a value near 120  $\Omega$ .

5. Implement this circuit in ADS and demonstrate that it is now unconditionally stable. If it is not, what would you do to fix that?

Figure 6 shows the result of adding a 120  $\Omega$  shunt resistor in the circuit. The circuit is now unconditionally stable.

6. Plot  $|S_{21}|$  and comment on the gain reduction compared to the original.

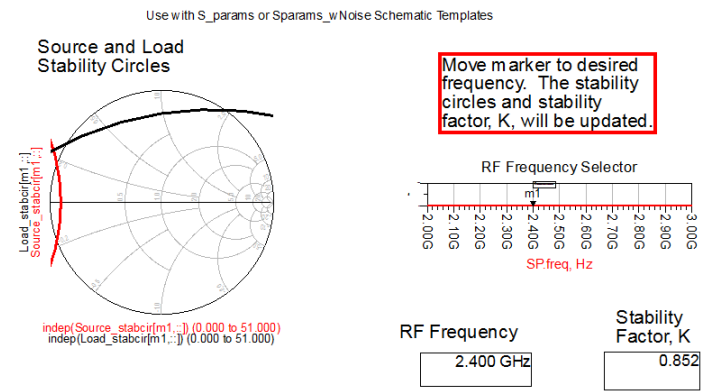


Fig. 5. Unoptimized stability circle at 2.4 GHz. The circuit is potentially unstable.

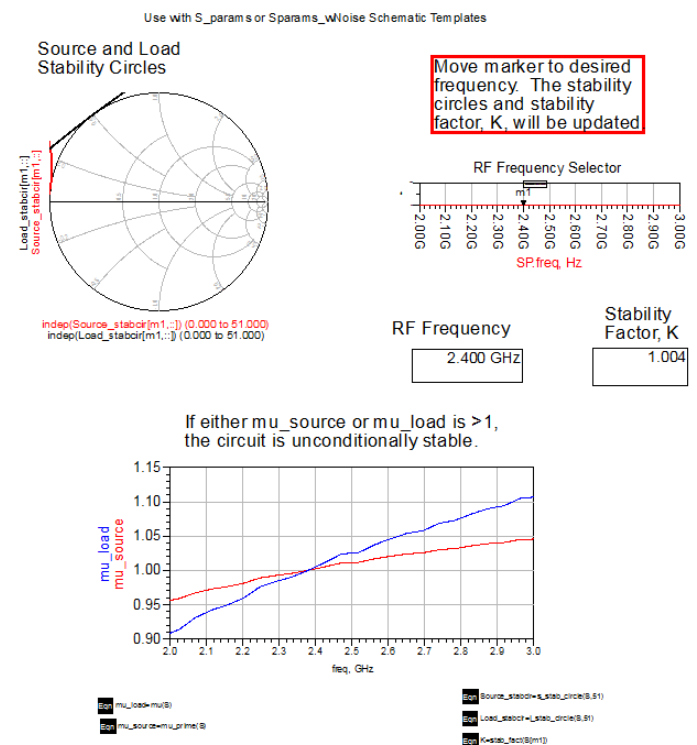


Fig. 6. Optimized stability circle at 2.4 GHz. The circuit is unconditionally stable.

Figure 7 shows the gain and the original gain on the same plot. The reduction is caused by adding the shunt

resistor.

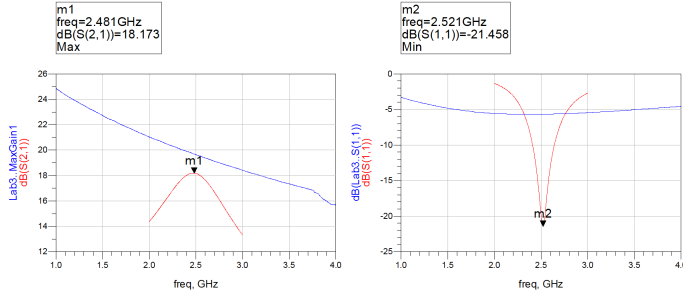


Fig. 7. Plot of original gain and the stabilized gain. Note the reduction in the stabilized gain plot.

### III. WEEKLY LESSONS

#### A. In-Class

**Stability Circles:** The region of stability on the I/O stability circle is determined by the magnitude of  $|S_{11}|$  and  $|S_{22}|$ . If  $|S_{11}|$  or  $|S_{22}| > 1$ , it is stable outside of the origin; if  $|S_{11}|$  or  $|S_{22}| < 1$  then it is stable inside the origin. Anything outside of the stable region is considered potentially unstable. In addition, to increase the stability region, a series/shunt resistor can be added to increase matching. However, the downfall of this is a lower gain, due to a non-trivial voltage drop across the stabilizing resistor.

#### B. Outside of Class

Fundamentals of testing RF amplifiers and high-power devices with RF VNA[1]: The Agilent webcast briefly reviewed S-Parameters and K (stability) factor. Then the talk discussed the Agilent E5072A VNA features including a built-in calculator (equation editor) that can be used to calculate parameters such as K and measuring high power output amplifiers using the direct receiver access (in addition to external components such as isolators/circulators). It covered gain compression measurements by using a booster amplifier (in combination with power receiver leveling) to sample a high-power input<sup>3</sup> applied to a DUT. Then it talked about measuring harmonic distortion (and intermodulation distortion) using Frequency-Offset Mode option which sweeps the input and output ports at different frequency ranges. It then discussed different configurations to measure high-power input to a DUT and high-power output from a DUT. Lastly, the webcast concluded the talk by explaining how to measuring specific applications such as RFID, SAW devices and antennas.

### REFERENCES

- [1] Agilent Webcast: <http://www.home.agilent.com/agilent/eventDetail.jsp?cc=US&lc=eng&ckey=2087011&nid=-11143.0.00&id=2087011>

<sup>3</sup>By high-power input this refers to an input signal that is higher than the analyzer can source